

Verilog Codes for Basic Digital Components

Combinational Logic

multiplexer (1/2)

```
module mux4_1 (  
  output reg out,  
  input i0, i1, i2, i3, s1, s0);  
  
  always @(*)  
  begin  
    case ({s1, s0})  
      2'd0 : out = i0;  
      2'd1 : out = i1;  
      2'd2 : out = i2;  
      2'd3 : out = i3;  
    end  
  
  endmodule
```

```
module mux4_1 (  
  output out,  
  input i0, i1, i2, i3, s1, s0);  
  
  assign out = s1 ? (s0 ? i3 : i2) : (s0 ? i1 : i0);  
  
endmodule
```

multiplexer (2/2)

```
// MUX3 with one-hot select
module MUX3_onehot (a2, a1, a0, s, b);
parameter k = 32;
input [k-1:0] a0, a1, a2;
input [2:0] s; // one-hot select
output [k-1:0] b;
reg [k-1:0] b;

always @ (*) begin
    case (s)
        3'b001: b = a0;
        3'b010: b = a1;
        3'b100: b = a2;
        default: b = {k{1'bx}};
    endcase
end
endmodule
```

```
// MUX3 with binary select
module MUX3_onehot (a2, a1, a0, s, b);
parameter k = 32;
input [k-1:0] a0, a1, a2;
input [1:0] s; // binary select
output [k-1:0] b;
reg [k-1:0] b;

always @ (*) begin
    case (s)
        0: b = a0;
        1: b = a1;
        2: b = a2;
        default: b = {k{1'bx}};
    endcase
end
endmodule
```

demultiplexer

```
module demux1_4 (  
  output reg out0, out1, out2, out3;  
  input in,  
  input [1:0] s );  
  
  always @(s, in0, in1, in2, in3)  
  case (s)  
    2'b00: begin out0 = in;   out1=1'bz; out2=1'bz; out3=1'bz; end  
    2'b01: begin out0 = 1'bz; out1=in;   out2=1'bz; out3=1'bz; end  
    2'b10: begin out0 = 1'bz; out1=1'bz; out2=in;   out3=1'bz; end  
    2'd11: begin out0 = 1'bz; out1=1'bz; out2=1'bz; out3=in;   end  
    default: $display ("Invalid control signals");  
  endcase
```

arbiter


```
// arbiter 4-bit wide
// LSB is highest priority
module Arb_4b_LSB (r, g);
output [3:0] r;
output [3:0] g;
reg [3:0] g;

always @ (*) begin
    casex (r)
        4'b0000: g = 4'b0000;
        4'bxxx1: g = 4'b0001;
        4'bxx10: g = 4'b0010;
        4'bx100: g = 4'b0100;
        4'b1000: g = 4'b1000;
        default: g = 4'bx;
    endcase
end
endmodule
```

```
// arbiter of arbitrary width: LSB is highest priority
```

```
module Arb_LSB (r, g);
parameter n=4;
input [n-1:0] r;
output [n-1:0] g;
wire [n-1:0]
c = { (~r[n-2:0] & c[n-2:0]), 1'b1 };

assign g = r & c;
endmodule
```

 

```
// arbiter of arbitrary width: MSB is highest priority
```

```
module Arb_MSB (r, g);
parameter n=4;
input [n-1:0] r;
output [n-1:0] g;
wire [n-1:0] c = { 1'b1, (~r[n-2:0] & c[n-2:0]) };

assign g = r & c;
endmodule
```

encoder

```
module encoder (  
    input i3, i2, i1, i0,  
    output reg [1:0] out);  
  
    always @(i3, i2, i1, i0)  
        valid = 1;  
    case ({i3, i2, i1, i0})  
        4'b1000: out = 2'b11;  
        4'b0100: out = 2'b10;  
        4'b0010: out = 2'b01;  
        4'b0001: out = 2'b00;  
    endcase  
  
endmodule
```

decoder (1/3)

```
module decoder (  
input [1:0] in;  
output reg out0, out1, out2, out3) ;  
  
always @(in)  
case (in)  
    2'b00: begin out0=1; out1=0; out2=0; out3=0; end  
    2'b01: begin out0=0; out1=1; out2=0; out3=0; end  
    2'b10: begin out0=0; out1=0; out2=1; out3=0; end  
    2'd11: begin out0=0; out1=0; out2=0; out3=1; end  
endcase  
  
endmodule
```


decoder (2/3)

```
module decoder_index (in1, out1);  
  parameter N=8;  
  paramete log2N = 3;  
  input [log2N-1: 0] in1;  
  output [N-1:0] out1;  
  
  always @ (in1) begin  
    out1 = 0;  
    out1[in1] = 1'b1;  
  end  
  
endmodule
```

```
module decoder_loop (in1, out1);  
  parameter N=8;  
  paramete log2N = 3;  
  input [log2N-1: 0] in1;  
  output reg [N-1:0] out1;  
  
  integer i;  
  
  always @ (in1)  
    for (i=0; i<N; i=i+1)  
      out1[i] = (in1 == i);  
  
endmodule
```

decoder (3/3)

```
// n-to-m decoder  
module Dec (a, b); parameter n=3;  
parameter m=8;  
input [n-1: 0] a;  
output [m-1:0] b;  
  
assign b = 1 << a;  
  
endmodule
```

priority encoder

```
module priority_enc42
(input i3, i2, i1, i0,
output reg [1:0] out;)

always @(i3, i2, i1, i0)
case ({i3, i2, i1, i0})
    4'b1xxx: out = 2'b11;
    4'b01xx: out = 2'b10;
    4'b001x: out = 2'b01;
    default : out = 2'b00;
endcase
```

```
// 8:3 priority encoder
module priority_enc83 (r, b);
input [7:0] r;
output [2:0] b;
reg [2:0] g;

assign b = g;
always @ (*) begin
    case®
        8'bxxxxxxx1: g = 0;
        8'bxxxxxx10: g = 1;
        8'bxxxxx100: g = 2;
        8'bxxxx1000: g = 3;
        8'bxxx10000: g = 4;
        8'bxx100000: g = 5;
        8'bx1000000: g = 6;
        8'b10000000: g = 7;
        default: g = x;
    endcase
end
endmodule
```

leading one detector

```
`define TRUE 1'b1;
`define FALSE 1'b0;

module LOD (
input [15:0] flag;
output integer i) ;

reg continue;

always
begin
i = 0; continue = `TRUE;
while ( i<16 && continue )
begin
if (flag[15-i]) continue = `FALSE;
i=i+1;
end
end
endmodule
```

```
// 8:3 reverse priority encoder
module reverse_priority_enc83 (r, b);
input [7:0] r;
output [2:0] b;
reg [2:0] g;

assign b = g;
always @ (*) begin
    casex®
        8'b1xxxxxxx: g = 0;
        8'b01xxxxxx: g = 1;
        8'b001xxxxx: g = 2;
        8'b0001xxxx: g = 3;
        8'b00001xxx: g = 4;
        8'b000001xx: g = 5;
        8'b0000001x: g = 6;
        8'b00000001: g = 7;
        default: g = x;
    endcase
end
endmodule
```

ripple carry adder

```
module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N-1:0] carry;

assign carry[0]=ci;

genvar i;
generate
    for (i=0; i<N; i=i+1)
        begin: r_loop
            wire t1, t2, t3;
            xor g1(t1, a0[i], a1[i]);
            xor g2(sum[i], t1, carry[i]);
            and g3(t2, a0[i], a1[i]);
            and g4(t3, t1, carry[i]);
            or g5(carry[i+1], t2, t3);
        end
    endgenerate

assign co = carry[N]

endmodule
```

left/right shifter

```
module shifter (  
input left,  
input [7:0] data_in, shift_amt,  
output [7:0] shifted_data);  
  
assign shifted_data = (left) ? data_in << shift_amt : data_in >> shift_amt;  
  
endmodule
```


wrap-around barrel shifter

```
module barrel_shift (n, a, b);  
  
    parameter k=8;  
    parameter lk=3;  
    input [lk-1:0] n;  
    output [k-1:0] b;  
  
    wire [2*k-2:0] x = a << n;  
  
    assign b = x[k-1 : 0] | {1'b0, x[2k-2 : k] };  
  
endmodule
```

ALU

```
module MIPSALU (  
  input [31:0] a, b;  
  input [3:0] ALU_ctl;  
  output reg [31:0] ALU_out;  
  output Zero );  
  
  assign Zero = (ALU_out == 0);  
  
  always @ (ALU_ctl, a, b)  
    case (ALU_ctl)  
      4'd0 : ALU_out = a & b;  
      4'd1 : ALU_out = a | b;  
      4'd 2 : ALU_out = a + b;  
      4'd6 : ALU_out = a - b;  
      4'd 7: ALU_out = (a < b) ? 1 : 0;  
      4'd12: ALU_out = ~(a | b);  
      default: ALU_out = 32'b0;  
    endcase  
  
endmodule
```

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

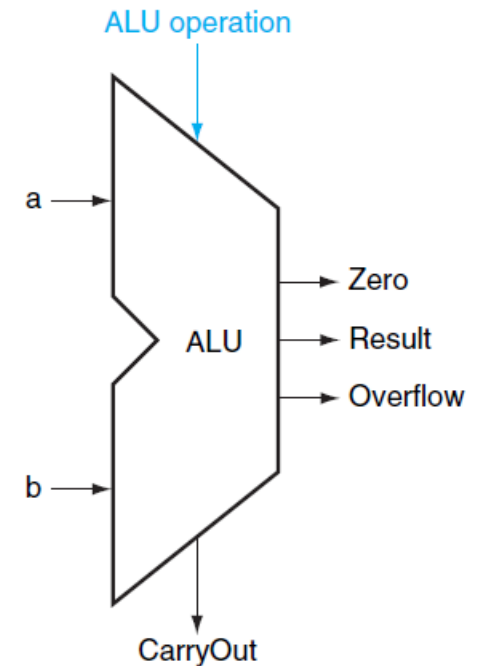


```

module rom_case (a, d) ;
  input [3:0] a;
  output [7:0] d;
  reg [7:0] d;
  always@(*) begin
    case(a)
      4'h0: d=8'h00;
      4'h1: d=8'h11;
      4'h2: d=8'h22;
      4'h3: d=8'h33;
      4'h4: d=8'h44;
      4'h5: d=8'h12;
      4'h6: d=8'h34;
      4'h7: d=8'h56;
      4'h8: d=8'h78;
      4'h9: d=8'h9a;
      4'ha: d=8'hbc;
      4'hb: d=8'hde;
      4'hc: d=8'hf0;
      4'hd: d=8'h12;
      4'he: d=8'h34;
      4'hf: d=8'h56;
      default: d=8'h0;
    endcase
  end
endmodule

```

ROM

```

module rom_reg (a, d) ;
  parameter b = 32;
  parameter w = 4;
  parameter fileName = "dataFile";
  input [w-1:0] a;
  output [b-1:0] d;
  reg [b-1:0] rom [2**w-1:0] ;
  initial begin
    $readmemb(fileName, rom);
  end
  assign d = rom[a];
endmodule

```

Sequential Logic

bus

```

module BusInt(cr_valid, cr_ready, cr_addr, cr_data, // bus rx - to the bus
             ct_valid, ct_data,                  // bus tx - from the bus
             br_addr, br_data, br_valid,         // to the bus
             bt_addr, bt_data, bt_valid,         // from the bus
             arb_req, arb_grant,                 // the arbiter
             my_addr) ;                          // address of this interface


parameter aw = 2 ; // address width
parameter dw = 4 ; // data width
input cr_valid, arb_grant, bt_valid ;
output cr_ready, ct_valid, arb_req, br_valid ;
input [aw-1:0] cr_addr, bt_addr, my_addr ;
output [aw-1:0] br_addr ;
input [dw-1:0] cr_data , bt_data ;
output [dw-1:0] br_data, ct_data ;

// arbitration
assign arb_req = cr_valid ;
assign cr_ready = arb_grant ;

// bus drive
assign br_valid = arb_grant ;
assign br_addr = arb_grant ? cr_addr : 0 ;
assign br_data = arb_grant ? cr_data : 0 ;

// bus receive
assign ct_valid = bt_valid & (bt_addr == my_addr) ;
assign ct_data = bt_data ;
endmodule


```

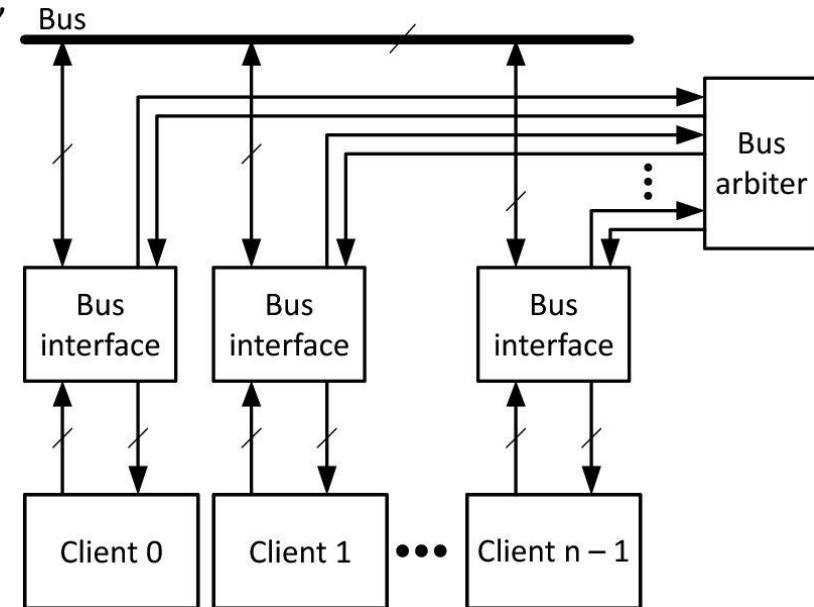

latch


```
module d_latch (  
  input gate, data,  
  output reg q );  
  
  always @ (gate or data)  
    if (gate) q <= data;  
  
endmodule
```
 
```
module d_CL (  
  input gate, data,  
  output reg q );  
  
  // infer a combinational logic  
  // not a latch  
  always @ (gate or data)  
    if (gate) q <= data;  
    else q <= 'b0;  
  
endmodule
```




latch with asynchronous set and reset
 
```
module d_latch_async (  
  input gate, data, reset_n, set_n;  
  output reg q;  
  
  always @ (gate, data, reset_n, set_n)  
    if (!set_n) q <= 1'b1;  
    else if (!reset_n) q <= 1'b0;  
    else if (gate) q <= data;  
  
endmodule
```



flip-flop
 
```
module dff (  
  input data, clk;  
  output reg q;  
  
  always @ (posedge)  
    q <= data;  
  
endmodule
```



DFF with asynchronous set and reset

```
module dff_async (  
  input clk, reset, set, data,  
  output reg q);
```


```
  always @ (posedge clk or posedge reset or posedge set)
```

```
    if (reset) q <= 1'b0;
```

```
    else if (set) q <= 1'b1;
```


```
    else q <= data;
```

```
endmodule
```

 


DFF with synchronous set
 
```
module dff_sync_set (  
  input data, clk, set;  
  output reg q;  
  
  always @ (posedge clk)  
    if (set) q <= 1'b1;  
    else q <= data;  
  
endmodule
```



DFF with synchronous reset
 
```
module dff_sync_reset (  
  input data, clk, reset_n;  
  output reg q;  
  
  always @ (posedge clk)  
    if (!reset_n) q<= 1'b0;  
    else q <= data;  
  
endmodule
```



register file

```
module RegisterFile (r_adr1, r_adr2, data1, data2, w_adr, w_data, w_cntl, clk)
input [5:0] r_adr1, r_adr2, w_adr;
input [31:0] w_data;
input w_cntl, clk;
output [31:0] data1, data2;
reg [31:0] RF [0:31];

assign data1 = RF[r_adr1];
assign data2 = RF[r_adr2];

always @ (posedge)
    if (w_cntl) RF[w_adr] = w_data;

endmodule
```

Pipeline


```
module pipelined (  
    input [31:0] A, B, C;  
    input clk;  
    output [63:0] );  
  
    reg [31:0] C_pipe1;  
    reg [63:0] out_pipe1, out_pipe2;  
  
    always @ (posedge clk) begin  
        out_pipe1 <= A*B;  
        C_pipe1 <= C;  
    end  
  
    always @(posedge clk)  
        out_pipe2 <= out_pipe1 + C_pipe1;  
  
    assign out = out_pipe2;  
  
endmodule
```

FSM

```
// lower section of FSM
always @ (posedge clk, posedge rst) begin
    if (rst == 1) pr_state <= ... ;
    else      pr_state <= nx_state;
    // out <= temp_out;  // for stored output
end

// upper section of FSM
always @ (pr_state, input) begin
case pr_state
    state1: begin
        tmp_out = ...;
        if ( input == ...) nx_state = ...; else nx_state = ...;
    end
    state2: ...
    ...
endcase
end

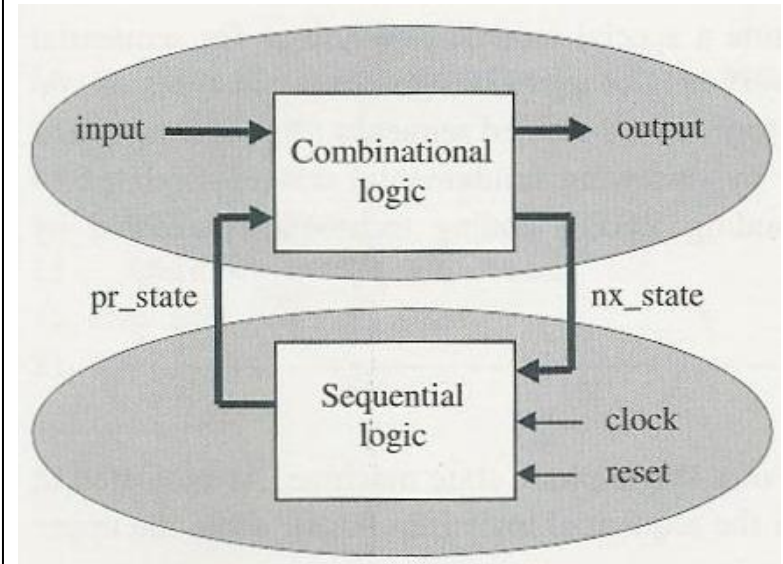// output section for not non-stored output
assign out = tmp_out;
```



shift register with parallel load

```
module shiftreg #(parameter N=32)
(input clk, reset, load, si,
input [0:N-1] d,
output [0:N-1] q,
output so);

always @(posedge clk)
if (reset) q <= 0;
else if (load) q <= d;
else {q, so} <= {si, q}

endmodule
```

left/right/load shift register

```

module LRL_Shift_Register(clk, rst, left, right,
load, sin, in, out) ;
    parameter n = 4 ;
    input clk, rst, left, right, load, sin ;
    input [n-1:0] in ;
    output [n-1:0] out ;
    reg [n-1:0] next ;

```

```


DFF #(n) cnt(clk, next, out) ;

```

```

always @(*) begin
    casex({rst,left,right,load})
        4'b1xxx: next = 0 ;           // reset
        4'b01xx: next = {out[n-2:0],sin} ; // left
        4'b001x: next = {sin,out[n-1:1]} ; // right
        4'b0001: next = in ;         // load
        default: next = out ;        // hold
    endcase
end
endmodule

```

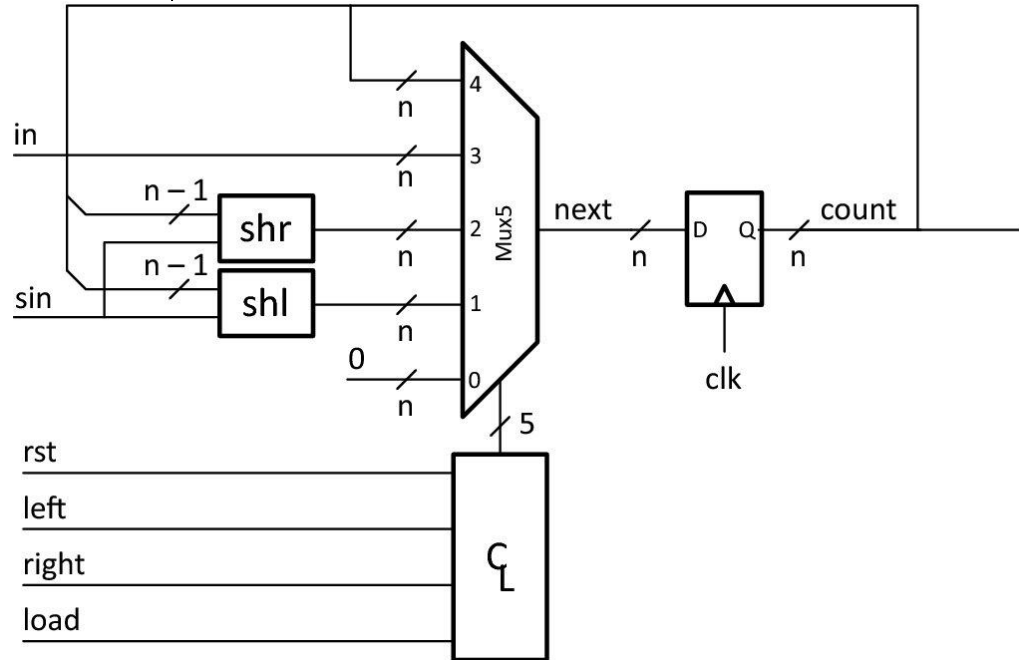

dual-port RAM

```
module RAM(ra, wa, write, din, dout) ;  
    parameter b = 32;  
    parameter w = 4;  
  
    input [w-1:0] ra, wa;  
    input      write;  
    input [b-1:0] din;  
    output [b-1:0] dout;  
  
    reg [b-1:0]    ram [2**w-1:0];  
  
    assign dout = ram[ra];  
  
    always@(*) begin  
        if(write == 1)  
            ram[wa] = din;  
    end  
endmodule
```

RAM with bidirectional data bus

```
module ram #(parameter N=6, M=32)
  (input clk, we,
   input [N-1:0] adr,
   inout [M-1:0] data);

  reg [M-1:0] mem [2**N-1:0];


  always @ (posedge clk)
    if (we) mem[adr] <= data;

  assign data = we ? 'z : mem[adr];

endmodule
```


clock gating
 
```
module dff(q, d, clk, set, rst);  
input d, clk, set, rst;  
output q;  
reg q;  
wire clk_en, en;  
  
// clock input is from the output of AND  
assign clk_en = clk & en;  
always @(posedge clk_en)  
if (rst)  
q <= 1'b0;  
else if (set)  
q <= 1'b1;  
else  
q <= d;  
endmodule
```



```
module dff(q, d, clk, set, rst);  
input d, clk, set, rst;  
output q;  
reg q;  
wire cen;  
  
// data input from MUX controlled by en  
always @(posedge clk)  
if (en) begin  
if (rst)  
q <= 1'b0;  
else if (set)  
q <= 1'b1;  
else  
q <= d;  
end  
endmodule
```

ROM

- one-dimensional array with data in case statement
- two-dimensional array with data in initial statement
- two-dimensional array with data in text file

ROM: 1D array using **case**

- Synthesis attribute *rom_block* model ROM

```
module rom_case(  
    (* synthesis, rom_block = "ROM_CELLXYZ01" *)  
    output reg [3:0] z,  
    input wire [2:0] a); // Address - 8 deep memory.  
  
    always @*          // @(a)  
        case (a)  
            3'b000: z = 4'b1011;  
            3'b001: z = 4'b0001;  
            3'b100: z = 4'b0011;  
            3'b110: z = 4'b0010;  
            3'b111: z = 4'b1110;  
            default: z = 4'b0000;  
        endcase  
endmodule // rom_case  
// z is the ROM, and its address size is determined by a.
```

ROM: 2D array using **initial**

- initial statement shall be supported when attributes *logic_block* or *rom_block* is used
- without specifying attributes, a synthesis tool may opt to implement either as random logic or as a ROM

```
module rom_2dimarray_initial (  
    output wire [3:0] z,  
    input wire [2:0] a); // address- 8 deep memory  
// Declare a memory rom of 8 4-bit registers. The indices are 0 to 7:  
(* synthesis, rom_block = "ROM_CELL XYZ01" *) reg [3:0] rom[0:7];  
// (* synthesis, logic_block *) reg [3:0] rom [0:7];  
  
    initial begin  
        rom[0] = 4'b1011;  
        rom[1] = 4'b0001;  
        rom[2] = 4'b0011;  
        rom[3] = 4'b0010;  
        rom[4] = 4'b1110;  
        rom[5] = 4'b0111;  
        rom[6] = 4'b0101;  
        rom[7] = 4'b0100;  
    end  
  
    assign z = rom[a];  
endmodule
```

ROM: 2D array with data in text file

```
module rom_2dimarray_initial_readmem (  
    output wire [3:0] z,  
    input wire [2:0] a);  
    // Declare a memory rom of 8 4-bit registers.  
    // The indices are 0 to 7:  
    (* synthesis, rom_block = "ROM_CELL XYZ01" *) reg [3:0] rom[0:7];  
  
    initial $readmemb("rom.data", rom);  
  
    assign z = rom[a];  
endmodule
```

```
// Example of content "rom.data" file:  
// file: /user/name/project/design/rom/rom.data  
// date : Jan 08, 02  
1011      // addr=0  
1000      // addr=1  
0000      // addr=2  
1000      // addr=3  
0010      // addr=4  
0101      // addr=5  
1111      // addr=6  
1001      // addr=7
```

RAM: 2D array using **always**

- in general, standard cell library vendors usually provide automatic generator (compiler) of memory, such as RAM, ROM, register file which are usually custom designs

```
// A RAM element is an edge-sensitive storage element:
module ram_test(
    output wire [7:0] q,
    input wire [7:0] d,
    input wire [6:0] a,
    input wire clk, we);
    (* synthesis, ram_block *) reg [7:0] mem [127:0];

    always @(posedge clk) if (we) mem[a] <= d;

    assign q = mem[a];
endmodule
```