

# Verilog: behavioral modeling, task and function

S. Palnitkar, “***Verilog HDL, A Guide to Digital Design and Synthesis***”, 2<sup>nd</sup> ed., , Sun Microsystems, Inc, 2003.

# Behavioral Modeling

# Procedural Assignments

- two structured procedures
  - **always** (SystemVerilog uses **always\_ff**, **always\_comb**)
  - **initial**
- procedural assignments update LHS values of
  - **reg** (SystemVerilog uses **logic**)
  - **integer**
  - **real**
  - **time**
- The value placed on a variable remain unchanged until another procedural assignment updates the variable with a different value
  - unlike continuous assignments (**assign**) in dataflow where one assignment can cause the value of RHS expression to be continuously placed on the LHS expression

# initial statement

- start at time 0, executes **exactly once** during a simulation, and then does not execute again.
- If there are multiple initial blocks, each block starts to execute **concurrently** at time 0
- Multiple sequential behavioral statements must be grouped using keywords **begin** and **end**
- typically used for initialization (for simulation, *not for design*), monitoring, waveforms, ...
  - Initial statement is NOT synthesizable, cannot be used to initialize values of DFF (instead, use synchronous or asynchronous set/reset, to be discussed later)




## **always** statement

- starts at time 0 and executes the statements in the always block continuously in a looping fashion
- used to model a block of activity that is repeated continuously in a digital circuit

```
module clock_gen (output reg clock);  
    initial clock = 1'b0;  
    always #10 clock = ~clock;  
    initial #1000 $finish;  
endmodule
```

# behavioral modeling

- Event-driven procedures: **always**, **initial**
- Sequential blocks: **begin...end**
- Parallel blocks: **fork...join**

```
module MyModule(...);  
    .  
    initial @ (...)   
    .  
    always @ (...)   
    .  
    always @ (...)   
    .  
endmodule
```

<pre>always @ (...)  begin → .   .   . End</pre>	<pre>initial @ (...)  begin → .   .   . end</pre>
<pre>always @ (...)  fork → . → . → . join</pre>	<pre>initial @ (...)  fork → . → . → . join</pre>

# behavioral statements

(used inside **initial** or **always** blocks)

- procedural assignments
  - blocking ( **=** ) vs. non-blocking ( **<=** )
- conditional statements (**if ... else...**)
- multi-way branching (**case ... endcase**)
- looping statement
  - **while, repeat, for, forever**
- sequential and parallel blocks
  - sequential block (**begin ... end**)
  - parallel block (**for ... join**)
- timing control (**#**)

# Blocking Assignments (=)

- executed in the order they are specified in a sequential block

```
reg x, y, z;
reg [15:0] reg_a, reg_b;
integer count;

initial begin
    x=0; y=1; z=1;           // scalar assignments
    count = 0;
    reg_a = 16'b0; reg_b = reg_a; // reg_b = 16'b0
#15 reg_a[2] = 1'b1;         // bit select assignment at time=15
# 10 reg_b[15:13] = {x,y,z}; // at time=25
    count = count + 1;       // at time=25
end
```



# Combinational logic using blocking statements (=)

- it is reasonable to describe *combinational logic* using blocking statements
  - model cascade of combinational logic gates

```
always @(in1 or in2)
begin
    a = in1 & in2;    // no assign keyword
    b = in1 | in2;
    {cout, sum} = a + b;
end
```

# Nonblocking Assignments (<=)

- allow scheduling of assignments without blocking execution of the statements that follow in a sequential block
  - typically, nonblocking assignments are executed last in the time step which they are scheduled, i.e., after all blocking assignments in the time step are executed

```
reg x, y, z;
reg [15:0] reg_a, reg_b;
integer count;
initial begin
    x=0; y=1; z=1;           // scalar assignments
    count = 0;
    reg_a = 16'b0; reg_b = reg_a;

    // the above statements are executed sequentially, but at time=0
    // the following statements are executed in parallel after
    reg_a[2]      <= #15 1'b1;    // bit select assignment at time=15
    reg_b[15:13] <= #10 {x,y,z};  // at time=10
    count        <= count +1;    // at time =0
end
```

# Application of nonblocking assignments

- modeling **concurrent** data transfers that take place after a common event

```
always @(posedge clock)
begin
    reg1 <= #1 in1;
    reg2 <= @(negedge clock) in2^in3;
    reg3 <= #1 reg1;    // the old value of reg1
end
```

1. a read operation is performed on each right-hand-side (RHS) variable at positive edge of the clock
2. the write operations to the left-hand-side variables (LHS) are scheduled to be executed according to delay control
3. the write operations are executed at the scheduled time

# 4-bit Shift register

## using nonblocking statements

- each flip-flop shift to its neighbor, except for the two boundary FFs that acts as input and output registers

```
always @(posedge clock)
begin
    reg1 <= d;
    reg2 <= reg1;
    reg3 <= reg2;
    out <= reg3;
end
```

# nonblocking assignments avoid race condition

```
// two concurrent always blocks with blocking statements
always @(posedge clk)
a = b;
always @(posedge clk)
b = a;
// either a=b are executed before b=a, or vice versa
// both registers will get same value (previous value of a or b)
```

```
// two concurrent always blocks with nonblocking statements
always @(posedge clk)
a <= b;
always @(posedge clk)
b <= a;
// at posedge clk, the values of all RHS variables are read,
// and stored in temporary variables, waiting to be evaluated
// reg a and reg b swap value
```

# emulate nonblocking using blocking


```
always @(posedge clk)  
begin  
  // read operations  
    temp_a = a;  
    temp_b = b;  
  // write operations  
    a = temp_b;  
    b = temp_a;  
end
```

```
always @(posedge clk)  
begin  
  a <= b;  
  b <= a;  
end
```
 
# synthesis of non-blocking and blocking


- non-blocking assignment (  $\leftarrow$  )

```
module rtl (clk, data, regc, regd);  
input data, clk;  
output regc, regd;  
  
reg regc, regd;  
  
always @(posedge clk)  
begin  
    regc <= data;  
    regd <= regc;  
end  
endmodule
```



- blocking assignment ( = )
 
```
module rtl (clk, data, rega, regb);  
input data, clk;  
output rega, regb;  
  
reg rega, regb;  
  
always @(posedge clk)  
begin  
    rega = data;  
    regb = rega;  
end  
endmodule
```



# Some rules of coding for `<=` and `=`

- In a procedural block (say **always**), never mix blocking (`=`) and non-blocking (`<=`) assignments
- For complicated *combinational* logic, use blocking assignments `=`
- Use non-blocking assignments `<=` for clocked *sequential* logic (with results stored in DFF)
- Never assign any data object in a module from more than one **always** block
  - Avoid race condition in *multiple assignment*
- DO NOT mix **level** and **edge** events in the sensitivity list of a procedural block
  - e.g. `always @ (posedge clk, negedge reset_n)` is good, but `always @ (posedge clk, reset_n)` is NOT good.



regular delay control ( **#T c=a+b; )**

**parameter** latency = 20;

**reg** x, y, z, p, q;

**begin**

x = 0 ; // no delay

**#10** y=1; // delay execution of y=1 by 10 units

**#(latency)** z=0;

**#(4:5:6)** q=0; // min, typical and max delays

**end**

# Intra-assignment delays ( **c = #T a+b;** )

```
reg x, y, z;
```

```
initial begin
```

```
x=0; z=0; // initialization of x and z at time=0
```

```
y= #5 x+z; // take values of x and z at time=0, evaluate x+z,  
           // and then wait for 5 time units to assign the value of x+z to y
```

```
end
```

```
/* equivalent method with temporary variables and regular delay control */
```

```
initial begin
```

```
x=0; z=0;
```

```
temp_xz = x+z; // x+z is executed at time=0
```

```
#5 y=temp_xz; // y is assigned the value of x+z at time=5
```

```
end
```

# regular event control

```
@(clk) q=d;
```

```
// q=d is executed when clk changes value
```

```
@(posedge clk) q=d;
```

```
// q=d is executed whenever clk does a
```

```
// positive transition (i.e., positive edge)
```

```
q = @(posedge clk) d;
```

```
// d is evaluated immediately,
```

```
// and assigned to q at the positive edge of clk
```

## named event control

```
// define an event called received_data
event received_data;
always @(posedge clk)
begin
// an event is triggered by the symbol ->
    if (last_data_packet) -> received_data;
end

// await triggering of event received_data
always @(received_data)
    data_buf={packet[0], packet[1], packet[2]};
```

# event OR control (sensitivity list)

```
// level-sensitive latch with asynchronous reset
always @ (rst or clk or d) // use or operator
begin
  if (rst) q=1'b0;           // if rst=1, set q to 0
  else if (clk) q=d;         // if clk is high, latch input
end
```

```
always @ (rst, clk, d)      // use comma (,) instead of or (IEEE 1364-2001)
begin
  if (rst) q=1'b0;
  else if (clk) q=d;
end
```

```
// a positive edge triggered D flip-flop with asynchronous falling reset
always @ (posedge clk, negedge rst_n)
if ( !rst_n) q <= 0;
else    q <= d;
```

## Use of @\*, or @(\*)

```
always @(a or b or c or d or e or f or g or h or p or m)
begin
out1 = a ? b+c: d+e;    // out1, out2 should be reg
out2 = f ? g+h: p+m;
end
```



// all input variables are included automatically

```
always @(*) // IEEE 1364-2001
```

```
begin
out1 = a ? b+c: d+e;
out2 = f ? g+h: p+m;
end
```
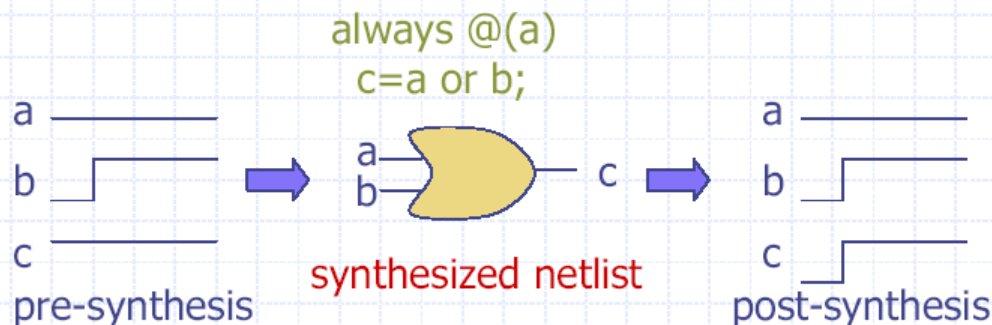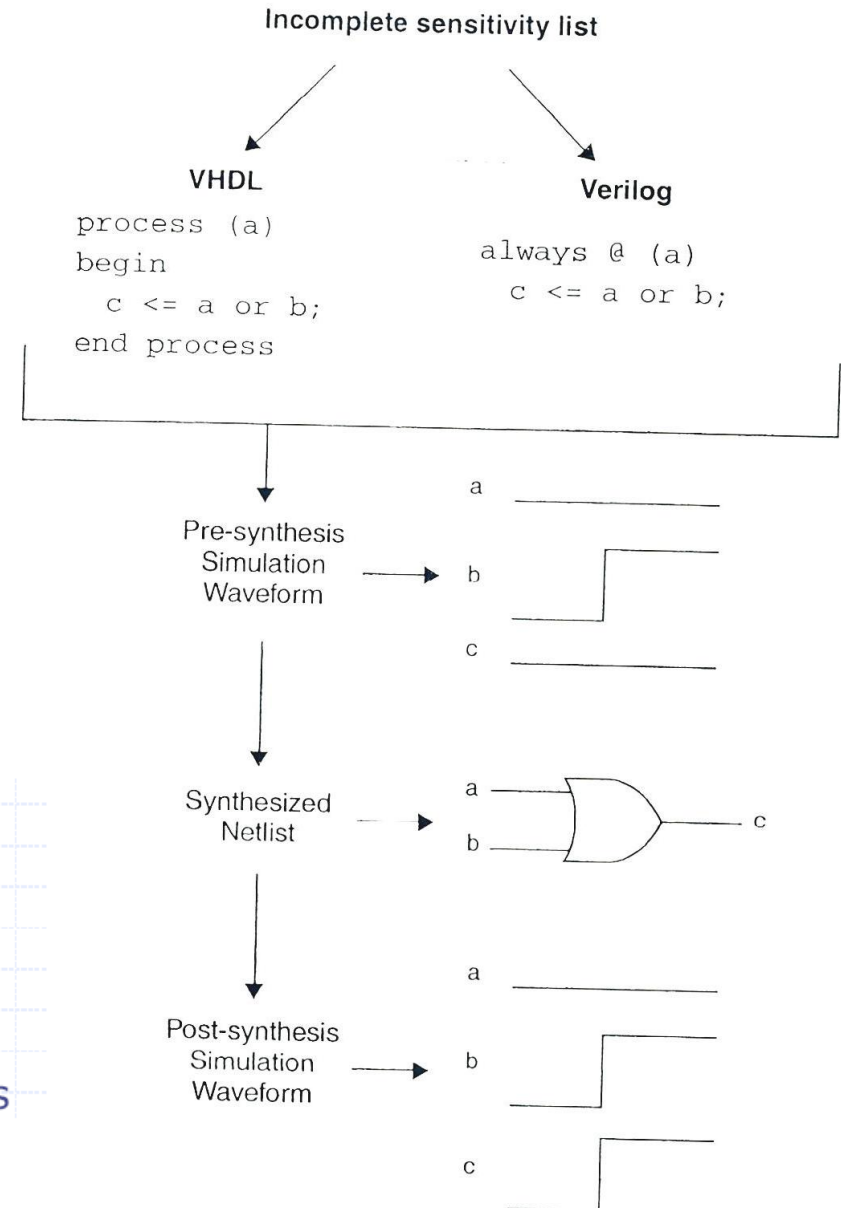
# simulation mismatch due to incomplete sensitivity list

- make sure your process sensitivity lists contain only necessary signals
- adding unnecessary sensitivity list slows down simulation



# Level-Sensitive Timing control

**always**

```
wait (count_enable) #20 count = count+1;  
// wait for count_enable = 1'b1  
// count will be incremented (with delay=20)  
// only when count_enable is at logic 1  
  
// cp. @ (event) ...  
// wait for the change of a signal value, or  
// for the triggering of an event
```



## conditional statements (**if ... else ...**)

```
if (!lock) buffer = data;  
if (enable) out = in; // infer a latch
```

```
if (number_queued < MAX_Q_DEPTH)  
    begin    data_queue = data;  
            number_queued = number_queued + 1;  
    end  
else  
    $display ("Queue Full. Try Again");
```

```
if (alu_control == 0)      y = x + z;  
else if (alu_control == 1) y = x - z;  
else if (alu_control == 2) y = x * z;  
else $display ("Invalid ALU control sign");
```

# Verilog vs. VHDL (conditional)

// Verilog

```
if (...)  
    begin ... ; end  
else if (...)  
    begin ...; end  
else if (...)  
    begin ...; end  
else  
    begin ...; end
```

-- VHDL

```
if (...) then  
...  
elsif (...) then  
...  
elsif (...) then  
...  
else  
...  
end if;
```

# Multiway Branching (Case Statements)

```
reg [1:0] alu_control;
```

```
...
```

```
case (alu_control)
```

```
    2'd0    : y = x + z;
```

```
    2'd1    : y = x - z;
```

```
    2'd2    : y = x * z;
```

```
    default : $display("Invalid ALU control signal");
```

```
endcase
```

# Verilog vs. VHDL (multi-way branching)

// Verilog

```
case ( )  
    ...      : begin ... end ;  
    ...      : begin ... end ;  
    default : begin ... end ;  
endcase;
```

-- VHDL

```
case ... is  
    when ...      => ... ;  
    when ...      => ... ;  
    when others => ... ;  
end case;
```

# 4-to-1 MUX with case

```
// 4-to-1 multiplexer (i1, i2, i3, s[1:0], out)
```

```
module mux4 (out, i0, i1, i2, i3, s0, s1);
```

```
output out;
```

```
input i0, i1, i2, i3, s0, s1;
```

```
reg out;
```

```
always @(s1, s0, i0, i1, i2, i3)
```

```
case ({s1, s0})
```

```
    2'd0: out = i0;
```

```
    2'd1: out = i1;
```

```
    2'd2: out = i2;
```

```
    2'd3: out = i3;
```

```
    default: $display ("Invalid control signals");
```

```
endcase
```

```
endmodule
```

# case statement with **x** and **z**

```
// 1-to-4 demultiplexer (in, s[1:0], out1, out2, out3, out4)
```

```
reg out0, out1, out2, out3;
```

```
always @ (s1 or s0 or in)
```

```
case ({s1, s0})
```

```
2'b00 : begin out0 = in;    out1 = 1'bz; out2=1'bz; out3=1'bz; end
```

```
2'b01 : begin out0 = 1'bz; out1 = in;    out2=1'bz; out3=1'bz; end
```

```
2'b10 : begin out0 = 1'bz; out1 = 1'bz; out2=in;    out3=1'bz; end
```

```
2'b11 : begin out0 = 1'bz; out1 = 1'bz; out2=1'bz; out3=in;    end
```

```
2'bx0, 2'bx1, 2'bxz, 2'bxx, 2'b0x, 2'b1x, 2'bx :
```

```
    begin out0=1'bx;  out1=1'bx;  out2=1'bx;  out3=1b'x; end
```

```
2'bz0, 2'bz1, 2b'zz, 2'b0z, 2'b1z :
```

```
    begin out0=1'bz;  out1=1'bz;  out2=1'bz;  out3=1b'z; end
```

```
default: $display (“unspecified control signals”);
```

```
endcase
```

# full case and parallel case

- full case
  - all possible branches are specified
  - otherwise, **latches** are synthesized
- parallel case
  - no cases overlap (one and only one of the branches is executed each time)
  - hardware multiplexers are synthesized in parallel case
  - if not determined, hardware *priority encoder* is synthesized (such as 1xxx, x1xx, xx1x, xxx1)

## both full case and parallel case

- a hardware multiplexer is synthesized

```
// full case, and parallel case  
// infer multiplexer
```

```
input [1:0] a;  
always @ (a, w, x, y, z) begin  
    case (a)  
        2'b11: b=w;  
        2'b10: b=x;  
        2'b01: b=y;  
        2'b00: b=z;  
    end
```



## parallel case, but not full case

- infer a latch for variable b to keep the value in cases that are not specified

```
// parallel case, but not full case
// infer a multiplexer with latched output b

input [1:0] a;
always @ (a, w, z) begin
    case (a)
        2'b11: b=w;
        2'b00: b=z;
    end
```

# casex, casez

- **casez**
  - treat all **z** values as don't care, **z** can also be represented by **?**
- **casex**
  - treat all **z** and **x** values as don't care

```
reg [3:0] encoding;  
integer state;
```

```
// not parallel case, but full case,  
// infer priority encoder
```

```
casex (encoding)
```

```
    4'b1xxx : next_state = 3;
```

```
    4'bx1xx : next_state = 2;
```

```
    4'bxx1x : next_state = 1;
```

```
    4'bxxx1 : next_state = 0;
```

```
    default : next_state = 0;
```

```
endcase
```

# 4-to-1 multiplexer (4:1 MUX)

- input
  - in0, in1, in2, in3, s[1:0]
- output
  - out

```
reg out;  
  
always @(s, in0, in1, in2, in3)  
case (s)  
    2'b00: out = in0;  
    2'b01: out = in1;  
    2'b10: out = in2;  
    2'd11: out = in3;  
    default: $display ("Invalid control signals");  
endcase
```

# 1-to-4 demultiplexer (1:4 DEMUX)

- input
  - in, s[1:0]
- output
  - out0, out1, out2, out3

```
reg out0, out1, out2, out3;
```

```
always @(s, in0, in1, in2, in3)
```

```
case (s)
```

```
2'b00: begin out0 = in;    out1=1'bz; out2=1'bz; out3=1'bz; end
```

```
2'b01: begin out0 = 1'bz; out1=in;    out2=1'bz; out3=1'bz; end
```

```
2'b10: begin out0 = 1'bz; out1=1'bz; out2=in;    out3=1'bz; end
```

```
2'd11: begin out0 = 1'bz; out1=1'bz; out2=1'bz; out3=in;    end
```

```
default: $display ("Invalid control signals");
```

```
endcase
```

## 4:2 priority encoder

- input
  - in0, in1, in2, in3
- output
  - out[1:0]

```
reg [1:0] out;  
  
always @(in3, in2, in1, in0)  
  casex ({in3, in2, in1, in0})  
    4'b1xxx: out = 2'b11;  
    4'b01xx: out = 2'b10;  
    4'b001x: out = 2'b01;  
    default : out = 2'b00;  
  endcase
```

## 4:2 encoder

- input
  - in0, in1, in2, in3
- output
  - out[1:0]

```
reg [1:0] out;  
reg      valid;  
  
always @(in3, in2, in1, in0)  
    valid = 1;  
    case ({i3, i2, i1, i0})  
        4'b1000: out = 2'b11;  
        4'b0100: out = 2'b10;  
        4'b0010: out = 2'b01;  
        4'b0001: out = 2'b00;  
        default : begin out = 2'bxx; valid = 0; end  
    endcase
```

## 2:4 decoder

- input
  - in[1:0]
- output
  - out0, out1, out2, out3

```
wire [1:0] in;  
reg out0, out1, out2, out3;  
  
always @(in)  
case (in)  
    2'b00: begin out0=1; out1=0; out2=0; out3=0; end  
    2'b01: begin out0=0; out1=1; out2=0; out3=0; end  
    2'b10: begin out0=0; out1=0; out2=1; out3=0; end  
    2'd11: begin out0=0; out1=0; out2=0; out3=1; end  
endcase
```

# while Loop

```
integer count;

initial
begin
count = 0;
while (count < 128)
    count = count + 1;
end
```

```
`define TRUE 1'b1;
`define FALSE 1'b0;
reg [15:0] flag;
integer i;
reg continue;

// find the leading 1 in flag
initial
begin
flag = 16'b 0010_0000_0000_0000
i = 0;
continue = `TRUE;
while ((i<16) && continue)
    begin
        if (flag[i]) continue = `FALSE;
        i=i+1;
    end
end
```



# for Loop

```
integer count;
```

```
initial
```

```
for (count=0; count<128; count=count+1)  
    $display("Count=%d", count);
```

```
`define MAX_STATES 32
```

```
integer state[0:MAX_STATES-1];
```

```
integer i;
```

```
initial
```

```
begin
```

```
for (i=0; i<32; i=i+2)
```

```
    state[i]=0;    //initialize even locations
```

```
for (i=1; i<32; i=i+2)
```

```
    state[i]=1;    //initialize odd locations
```

```
end
```

# repeat Loop

- repeat construct must contain a number

```
integer count;

initial
begin
count=0;
repeat (128)
begin
    count = count+1;
end
end
```

```
module data_buffer(data_start, data, clk);
parameter cycles=8;
input data_start;
input [15:0] data;
input clk;
reg [15:0] buffer[0:7];
integer i;

always @(posedge clk) begin
    if (data_start) begin
        i=0;
        // store data at next 8 clock edges
        repeat (cycles)
            begin
                // wait till next posedge to latch data
                @(posedge clk) buffer[i]=data;
                i=i+1;
            end
        end
    end
end
endmodule
```

# forever loop


- execute forever until the **\$finish** task

```
// clock generation using  
// forever loop instead of  
// always block  
reg clk;  
  
initial  
begin  
clk=1'b0;  
forever #10 clk=~clk;  
end
```

```
// synchronize two register values  
// at every positive edge of clk  
reg clk;  
reg x, y;  
  
initial  
forever @(posedge clk) x = y;
```
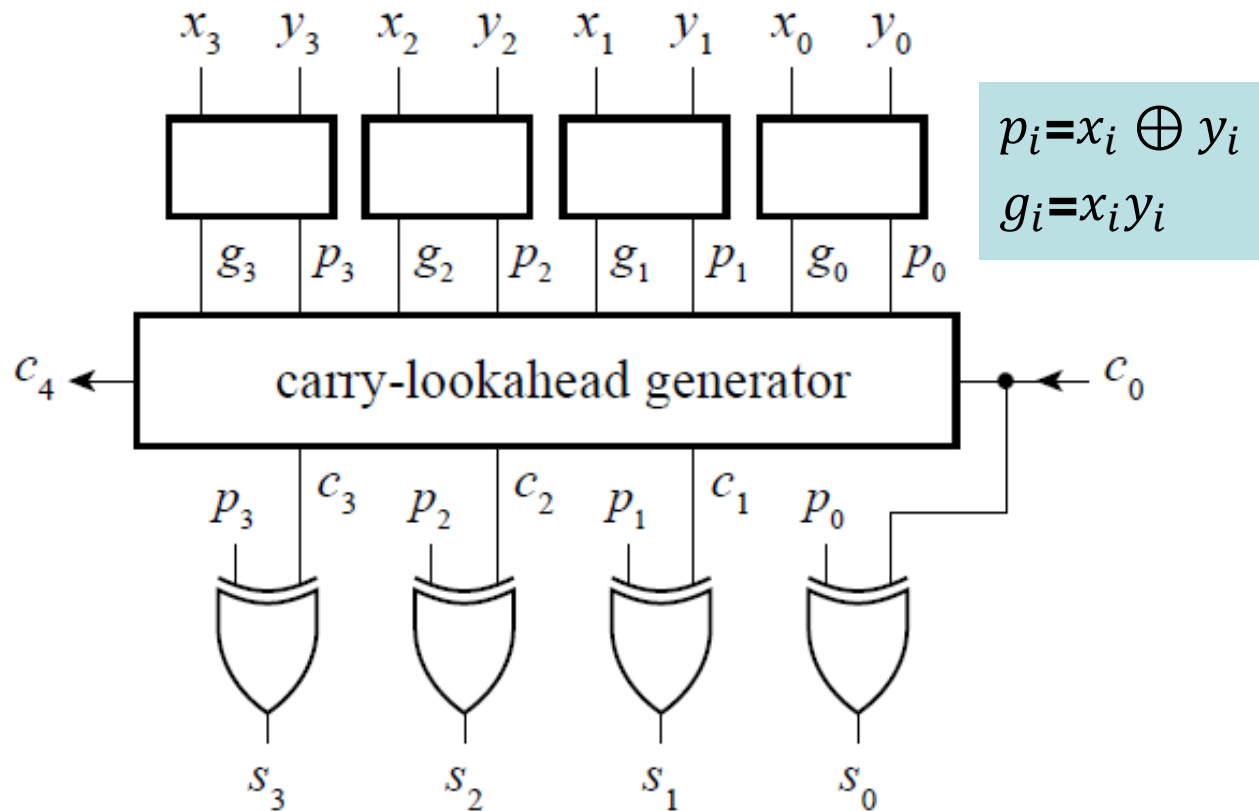
# Example: Carry Lookahead Adder

- 4-bit CLA
  - propagate  $p_i$
  - generate  $g_i$



$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + c_0 p_0$$

$$c_2 = g_1 + c_1 p_1 = g_1 + g_0 p_1 + c_0 p_0 p_1$$

$$c_3 = g_2 + c_2 p_2 = g_2 + g_1 p_2 + g_0 p_1 p_2 + c_0 p_0 p_1 p_2$$

$$c_4 = g_3 + c_3 p_3 = g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3 + c_0 p_0 p_1 p_2 p_3$$

# Example (16-bit carry lookahead adder)

$$G_{3:0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{3:0} = p_3 p_2 p_1 p_0$$

$$G_{7:4} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

$$P_{7:4} = p_7 p_6 p_5 p_4$$

...

$$G_{11:8} = \dots, P_{11:8} = \dots$$


$$G_{15:12} = \dots, P_{15:12} = \dots$$

$$c_4 = G_{3:0} + P_{3:0} c_0$$

$$c_8 = G_{7:4} + P_{7:4} c_4$$

$$c_{12} = G_{11:8} + P_{11:8} c_8$$
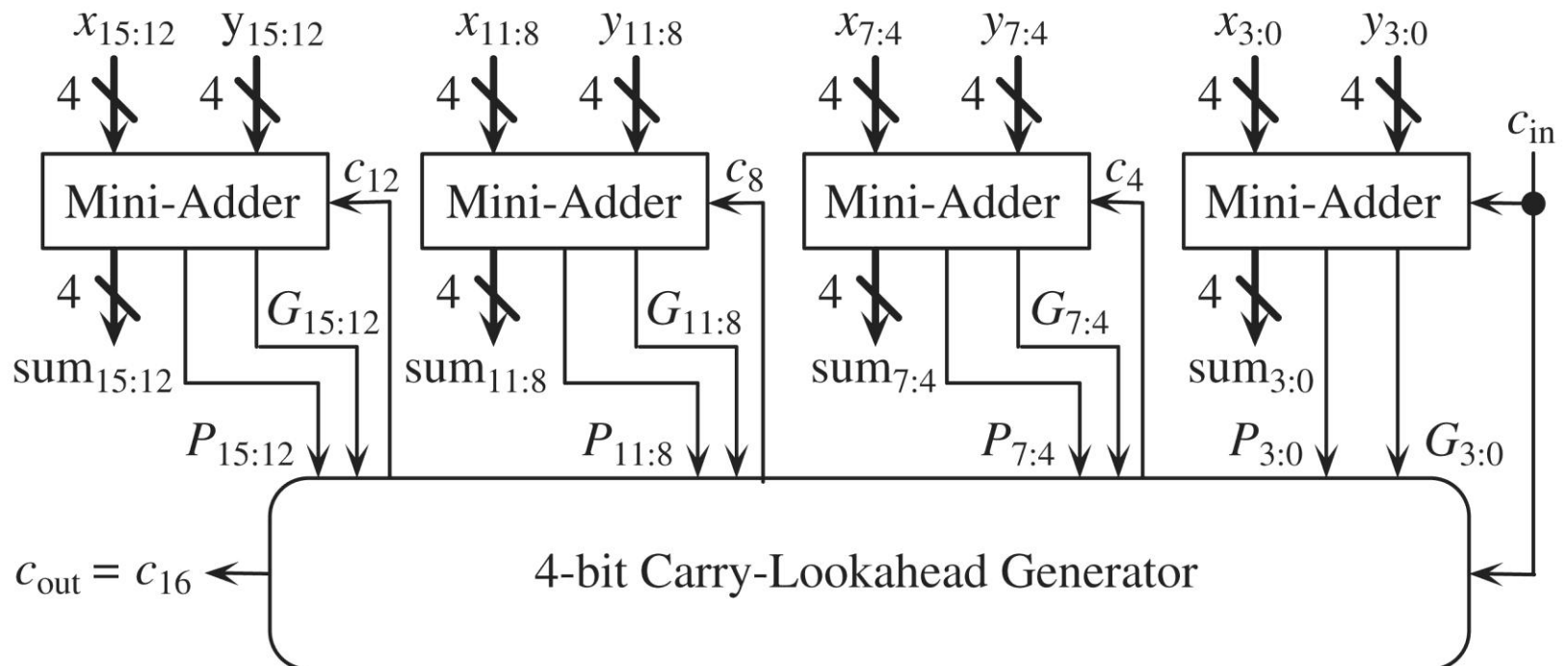
$$c_{16} = G_{15:12} + P_{15:12} c_{12}$$



# Carry Look Ahead (CLA) Adder

**propagate** and **generate** signals:

$$p_i = x_i + y_i \quad (p_i = \overline{x_i \oplus y_i})$$

$$g_i = x_i y_i$$

$$c_{i+1} = g_i + p_i c_i$$

**Group** propagate and generate:

$$G_{3:0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{3:0} = p_3 p_2 p_1 p_0$$

$$G_{7:4} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

$$P_{7:4} = p_7 p_6 p_5 p_4$$

$$c_i = g_i + p_i c_{i-1}$$

$$= g_i + p_i (g_{i-1} + p_{i-1} c_{i-2})$$


$$= g_i + p_i (g_{i-1} + p_{i-1} (g_{i-2} + p_{i-2} c_{i-3}))$$

$$= g_i + p_i (g_{i-1} + p_{i-1} (g_{i-2} + p_{i-2} (g_{i-3} + p_{i-3} c_{i-3})))$$

$$= \mathbf{g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + p_i p_{i-1} p_{i-2} g_{i-3} + p_i p_{i-1} p_{i-2} p_{i-3} c_{i-3}}$$

$$= \mathbf{G_{i:i-3} + P_{i:i-3} c_{i-3}}$$

$x_i$	$y_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	1	1

 

# 16-bit p\_g\_generator with 4-bit p\_g block (1/2)

```
`define DATA_BITS 16 // number of bits in input and output data
`define NUM_GROUPS 4  // number of stages (or groups) used
`define GROUP_BITS (`DATA_BITS / `NUM_GROUPS) // bits in 1 stage
```

```
// MODULE DECLARATION
```

```
module p_g_generator (P, G, a, b);
```

```
    output [`NUM_GROUPS-1:0] P; // group-propagate signals
```

```
    output [`NUM_GROUPS-1:0] G; // group-generate signals
```

```
    input  [`DATA_BITS-1:0] a, b; // adder inputs
```

```
// SIGNAL DECLARATIONS
```

```
    reg [`NUM_GROUPS-1:0] P;    // group-propagate signals
```

```
    reg [`NUM_GROUPS-1:0] G;    // group-generate signals
```

```
    reg [`DATA_BITS-1:0] p;     // propagate signals
```

```
    reg [`DATA_BITS-1:0] g;     // generate signals
```

```
    integer i, j;              // indices used in for loops
```

# 16-bit p\_g\_generator with 4-bit p\_g block (2/2)

// always block used to model combinational logic

**always @ (a or b) begin**

**for** (i = 0; i < `NUM\_GROUPS; i = i + 1) **begin**

P[i] = 1;

G[i] = 0;

**for** (j = `GROUP\_BITS-1; j >= 0; j = j - 1) **begin**

p[i\*`GROUP\_BITS+j] = (a[i\*`GROUP\_BITS + j] | b[i\*`GROUP\_BITS + j]);

g[i\*`GROUP\_BITS+j] = (a[i\*`GROUP\_BITS + j] & b[i\*`GROUP\_BITS + j]);

G[i] = G[i] | (g[i\*`GROUP\_BITS+j] & P[i]);

P[i] = P[i] & p[i\*`GROUP\_BITS+j];

**end**

**end**

**end**

**endmodule**

$$G_{3:0} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$P_{3:0} = p_3 p_2 p_1 p_0$$

$$G_{7:4} = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

$$P_{7:4} = p_7 p_6 p_5 p_4$$

...

$$G_{11:8} = \dots, P_{11:8} = \dots$$

$$G_{15:12} = \dots, P_{15:12} = \dots$$



# 16-bit Hierarchical CLA (1/3)

```
`define DATA_BITS 16 // number of bits in input and output data
`define NUM_GROUPS 4 // number of stages (or groups) used
`define GROUP_BITS (`DATA_BITS / `NUM_GROUPS) // bits in 1 stage
```

// MODULE DECLARATION

```
module hierarchical_cla_adder (sum, cout, x, y, cin);
```

```
    output [`DATA_BITS-1:0] sum; // the resulting sum value
```

```
    output cout;           // carry-out bit
```

```
    input [`DATA_BITS-1:0] x, y; // the two numbers to be added
```

```
    input cin;             // carry-in to the adder
```

// Declaration of "reg" outputs

```
    reg [`DATA_BITS-1:0] sum;
```

```
    reg cout;
```

// Declaration of internal signals


```
    reg [`DATA_BITS:0] carry; // intermediate carry signals
```

```
    reg [`NUM_GROUPS-1:0] temp; // temporary signal
```

```
    wire [`NUM_GROUPS-1:0] GP; // group propagate signals
```

```
    wire [`NUM_GROUPS-1:0] GG; // group generate signals
```
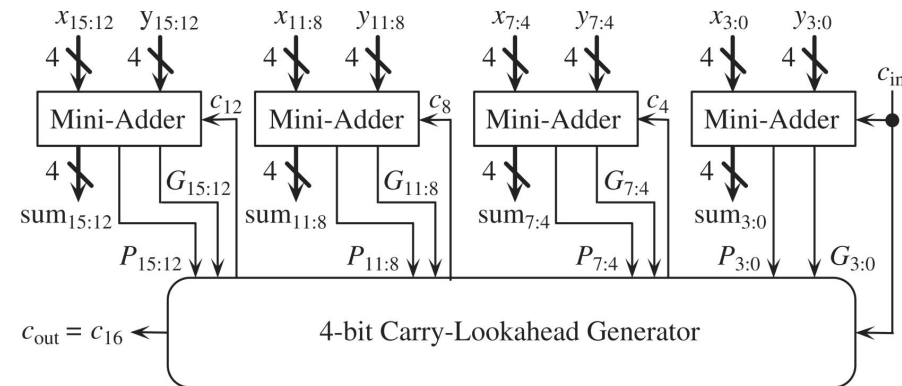
```
    integer i, j;           // indices used in for loops
```



# 16-bit Hierarchical CLA (2/3)

// use a lower-level block for GP[i] and GG[i] signals

p\_g\_generator UNIT0 (GP, GG, x, y);

// create the carry-lookahead logic and ripple-carry adders

**always** @ (x or y or GP or GG or cin) **begin**

// first describe carry-lookahead generation block

carry[0] = cin;

**for** (i = 0; i < `NUM\_GROUPS; i = i + 1) **begin**

carry[(i+1)\*`GROUP\_BITS] = GG[i];

carry[(i+1)\*`GROUP\_BITS] = carry[(i+1)\*`GROUP\_BITS] | (GP[i] & carry[i\*`GROUP\_BITS]);

**end** // of for (i)

cout = carry[`NUM\_GROUPS \* `GROUP\_BITS];

$G_{3:0}, P_{3:0}$

$G_{7:4}, P_{7:4}$

$G_{11:8}, P_{11:8}$


$G_{15:12}, P_{15:12}$

$$c_4 = G_{3:0} + P_{3:0}c_0$$

$$c_8 = G_{7:4} + P_{7:4}c_4$$

$$c_{12} = G_{11:8} + P_{11:8}c_8$$

$$c_{16} = G_{15:12} + P_{15:12}c_{12}$$

 

# 16-bit Hierarchical CLA (3/3)

// next, generate the ripple-carry adder stages

```

for (i = 0; i < `NUM_GROUPS; i = i + 1) begin
  for (j = 0; j < (`GROUP_BITS-1); j = j + 1) begin
    {carry[i*`GROUP_BITS + j + 1], sum[i*`GROUP_BITS + j]} =
      x[i*`GROUP_BITS + j] + y[i*`GROUP_BITS + j] +
      carry[i*`GROUP_BITS + j];
  end // of for (j)
  {temp[i], sum[(i+1)*`GROUP_BITS - 1]} =
    x[(i+1)*`GROUP_BITS - 1] + y[(i+1)*`GROUP_BITS - 1] +
    carry[(i+1)*`GROUP_BITS - 1];
end // of for (i)

end // of always block
endmodule
  
```


**// use 4-bit RCA**

$\{c_1, s_0\} = x_0 + y_0 + c_0$   
 $\{c_2, s_1\} = x_1 + y_1 + c_1$   
 $\{c_3, s_2\} = x_2 + y_2 + c_2$   
 $\{c_5, s_4\}, \{c_6, s_5\}, \{c_7, s_6\}$   
 $\{c_9, s_8\}, \{c_{10}, s_9\}, \{c_{11}, s_{10}\}$   
 $\{c_{13}, s_{12}\}, \{c_{14}, s_{13}\}, \{c_{15}, s_{14}\}$

**//**  $c_4, c_8, c_{12}, c_{16}$  been calculated  
 $\{temp, s_3\} = x_3 + y_3 + c_3$   
 $\{temp, s_7\} = x_7 + y_7 + c_7$   
 $\{temp, s_{11}\} = x_{11} + y_{11} + c_{11}$   
 $\{temp, s_{15}\} = x_{15} + y_{15} + c_{15}$

 **// use 4-bit CLA**

$c_1 = g_0 + p_0 c_0$   
 $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_{i-2}$   
 $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$   
 ...



## Sequential Blocks (**begin ... end**)

- the statements are processed in the order they are specified
  - except for *non-blocking assignments* (**<=**) with intra-assignment timing control
- delay or event control is relative to the simulation time when the *previous statement* completed execution

# Examples (Sequential Block)

```
// sequential block
// without delay
reg x, y;
reg [1:0] z, w;
initial
begin
    x=1'b0;
    y=1'b1;
    z={x,y}; // z=01
    w={y,x}; // w=10
end
```

```
// sequential block with delay
reg x, y;
reg [1:0] z, w;
initial
begin
    x=1'b0; // complete at time=0
    #5 y =1'b1; // complete at time=5
    #10 z={x,y}; // complete at time=15
    #20 w={y,x}; // complete at time=35
end
```

## Parallel Blocks (**fork ... join**)

- statements are executed concurrently
- ordering of statements is controlled by the delay or event control
- delay or event control is relative to the time the block was entered

# Examples (Parallel Blocks)

```
reg x, y;    reg [1:0] z, w;  
initial  
fork  
    x=1'b0;    // complete at time=0  
#5  y=1'b1;    // complete at time=5  
#10 z={x,y};   // complete at time=10  
#20 w={y,x};   // complete at time=20  
join
```

// race condition, values of z and w are non-deterministic

```
reg x, y;    reg [1:0] z, w;  
initial  
fork  
    x=1'b0;  
    y=1'b1;  
    z={x,y}; // z is unknown  
    w={y,x}; // w is unknown  
join
```

# Named Block

```
module top;
```

```
initial
```

```
begin: block1    // sequential block named block1  
    integer i;    // integer i is static and local to block1,  
                  // can be accessed by hierarchical name, top.block1.i
```

```
    ....
```

```
end
```

```
initial
```

```
fork: block2    // parallel block named block2  
    reg i;        // register i is static and local to block 2  
                  // can be accessed by hierarchical name, top.block2.i
```

```
    ...
```

```
join
```

```
endmodule
```



# Disabling Named Block

```
reg [15:0] flag;  
integer i;  
initial  
begin  
flag = 16'b 0010_0000_0000_0000;  
i = 0;  
  
begin: block1  
while (i<16) begin  
    if (flag[i]) begin  
        $display("encountered a TRUE bit at element number %d", i);  
        disable block1;  
    end  
    i=i+1;  
end  
end  
  
end
```

# generate blocks

- allow Verilog code to be generated *dynamically* at the elaboration time (before simulation)
- help the creation of parameterized models
- applications
  - same operation or module instance is repeated
    - eg., 64-b ripple carry adder (cascaded of 64 FA cells)
  - certain Verilog code is conditionally included based on parameter definitions
    - eg., Booth or non-Booth multiplier based on bit-width

# generate loop

- allow multiple instantiation
- note that generate should be used **outside** of procedural blocks (**always**, **initial**)

```
module bitwise_xor(out, i0, i1);  
parameter N=32;  
output [N-1:0] out;  
input [N-1:0] i0, i1;  
  
genvar j; // var. j is local  
generate  
    for (j=0; j<N; j=j+1)  
        begin: xor_loop  
            xor g(out[j], i0[j], i1[j]);  
        end  
// hierarchical name referencing:  
// xor_loop[0].g, xor_loop[1].g, ...,  
endgenerate  
  
endmodule
```

```
// alternate style (behavioral level)  
reg [N-1:0] out;  
  
genvar j;  
generate  
    for (j=0; j<N; j=j+1)  
        begin: bit  
            always @ (i0[j] or i1[j])  
                out[j] = i0[j] ^ i1[j];  
        end  
endgenerate
```

# Discussion of generate block

- before simulation, simulator elaborates (unrolls) the code in the generate blocks
- then, the unrolled code is simulated
  - a convenient way of replacing multiple repetitive Verilog statements with a single statement inside a loop
- **genvar** is to declare variables used in generate block, do not exist in simulation
- hierarchical name referencing:  
xor\_loop[0].g, xor\_loop[1].g, ..., xor\_loop[31].g

# generated ripple adder

```
module ripple_adder(co, sum, a0, a1, ci);  
parameter N=4;  
output [N-1:0] sum;  
output co;  
input [N-1:0] a0, a1;  
input ci;  
wire [N-1:0] carry;
```

```
assign carry[0]=ci;
```

```
genvar i;
```

```
generate
```

```
    for (i=0; i<N; i=i+1)
```

```
        begin: r_loop
```

```
            wire t1, t2, t3;
```

```
            xor g1(t1, a0[i], a1[i]);
```

```
            xor g2(sum[i], t1, carry[i]);
```

```
            and g3(t2, a0[i], a1[i]);
```

```
            and g4(t3, t1, carry[i]);
```

```
            or g5(carry[i+1], t2, t3);
```

```
        end
```

```
endgenerate
```

```
assign co = carry[N]
```

```
endmodule
```

# generate conditional

```
module multiplier (product, a0, a1);  
// 8-bit bus by default,  
// could be changed during instantiation using defparam or #  
parameter a0_width = 8;  
parameter a1_width = 8;  
  
// the following parameter cannot be modified using defparam  
localparam product_width = a0_width + a1_width;  
  
output [product_width-1:0] product;  
input [a0_width-1:0] a0;  
input [a1_width-1:0] a1;  
  
generate  
    if (a0_width < 8) || (a1_width < 8)  
        cla_multiplier #(a0_width, a1_width) m0 (product, a0, a1);  
    else  
        tree_multiplier #(a0_width, a1_width) m0 (product, a0, a1);  
endgenerate  
endmodule
```

# generate case

```
module adder (co, sum, a0, a1, ci);  
parameter N=4;  
output [N-1:0] sum;  
output co;  
input [N-1:0] a0, a1;  
input ci;  
generate  
    case (N)  
        1 : adder_1bit      adder1(co, sum, a0, a1, ci);  
        2 : adder_2bit      adder2(co, sum, a0, a1, ci);  
        default : adder_cla #(N) adder3(co, sum, a0, a1, ci);  
    endcase  
endgenerate  
endmodule
```

# Tasks and Functions



# Tasks vs. Functions

- task is similar to subroutine in FORTRAN
- function is similar to function in FORTRAN

Table 8-1 Tasks and Functions

Functions	Tasks
A function can enable another function but not another task.	A task can enable other tasks and functions.
Functions always execute in 0 simulation time.	Tasks may execute in non-zero simulation time.
Functions must not contain any delay, event, or timing control statements.	Tasks may contain delay, event, or timing control statements.
Functions must have at least one <b>input</b> argument. They can have more than one <b>input</b> .	Tasks may have zero or more arguments of type <b>input</b> , <b>output</b> , or <b>inout</b> .
Functions always return a single value. They cannot have <b>output</b> or <b>inout</b> arguments.	Tasks do not return with a value, but can pass multiple values through <b>output</b> and <b>inout</b> arguments.

# Tasks vs. Functions

- defined in a module and local to the module
  - contain *behavioral statements only*
  - called from **always** or **initial** blocks, or other tasks and functions
- tasks are used for commonly Verilog code
  - contain delays, timing, event constructs, or multiple output arguments
  - can have input, output and inout arguments
- functions are used for code that
  - is purely **combinational**
  - executes in zero simulation time
  - provides exactly one output
  - can have input arguments

# Tasks (task ... endtask)

```
module operation;
...
parameter delay=10;
reg [15:0] A, B;
reg [15:0] AB_AND, AB_OR, AB_XOR;
always @ (A or B)
begin
    bitwise_oper(AB_AND, AB_OR, AB_XOR,
        A, B);
end
...
task bitwise_oper;
output [15:0] ab_and, ab_or, ab_xor;
input [15:0] a, b;
begin
    #delay ab_and = a & b;
    ab_or = a | b;
    ab_xor = a ^ b;
end
end task
...
endmodule
```

```
// another task declaration
//
task bitwise_oper (
    output [15:0] ab_and, ab_or, ab_xor,
    input [15:0] a, b);
begin
    #delay ab_and = a & b;
    ab_or = a | b;
    ab_xor = a ^ b;
end
endtask
```

# Example: Asymmetric Sequence Generator

```
module sequence;  
reg clk;  
initial init_sequence;           // invoke task init_sequence  
always asymmetric_sequence; // invoke another task  
  
task init_sequence; begin  clk= 1'b0; end endtask  
  
task asymmetric_sequence; begin  
#12 clk = 1'b0;  
#5  clk = 1'b1;  
#3  clk = 1'b0;  
#10 clk = 1'b;  
end endtask  
  
endmodule
```

# Automatic (Re-entrant) Tasks

// all normally declared task items are *statically* allocated and shared.  
// automatic task allows for *dynamic* allocation for each invocation  
// where each task call operates in an independent space.

```
module top;  
reg [15:0] cd_xor, ef_xor;  
reg [15:0] c, d, e, f;
```

```
task automatic bitwise_xor;  
output [15:0] ab_xor;  
input [15:0] a, b;  
begin  
#delay ab_and = a & b;  
ab_or = a | b;  
ab_xor = a ^ b;  
end endtask
```

```
// two tasks are called concurrently in two procedural blocks  
always @(posedge clk) bitwise_xor (ef_xor, e, f);  
always @(posedge clk2) bitwise_xor (cd_xor, c, d); // clk2 twice frequency  
endmodule
```

# Function (**function** ... **endfunction**)

```
module parity;  
reg [31:0] addr;  
reg parity;  
always @(addr)  
    parity = calc_parity(addr);
```

```
function calc_parity;  
input [31:0] address;  
begin  
    calc_parity = ^address;  
end  
endfunction
```

```
endmodule
```

```
// alternate function definition  
function calc_parity  
    (input [31:0] address);  
begin  
    calc_parity = ^address;  
end  
endfunction
```

# Example: Left/Right Shifter

```
module shifter;  
  'define LEFT_SHIFT 1'b0;  
  'define RIGHT_SHIFT 1'b1;  
  reg [31:0] addr, left_addr, right_addr;  
  reg control;  
  always @(addr)  
  begin  
    left_addr = shift (addr, 'LEFT_SHIFT);  
    right_addr = shift (addr, 'RIGHT_SHIFT);  
  end
```

```
function [31:0] shift; // function output is a 32-bit value
```

```
input [31:0] address;
```

```
input control;
```

```
begin
```

```
shift = (control == 'LEFT_SHIFT) ? (address << 1) : (address >> 1);
```

```
end
```

```
endfunction
```

```
endmodule
```

# Automatic (Recursive) Functions

// functions are normally used non-recursively  
// automatic function allows all function declarations allocated dynamically  
// for each recursive call  
// each call to an automatic function operates in an independent variable space.

**module** top;

**function automatic** integer factorial;

**input** [31:0] oper;

**integer** i;

**begin**

**if** (oper >= 2 ) factorial = **factorial**(oper-1) \* oper;

**else** factorial = 1;

**end** **endfunction**

**integer** result;

**initial** result = factorial(4);

**endmodule**



# Constant Function

```
module ram (...);  
parameter RAM_DEPTH = 256;  
input [ clogb2(RAM_DEPTH) - 1 : 0] addr_bus;  
  
function integer clogb2 (input integer depth);  
begin  
for (clogb2=0; depth >0; clogb2=clogb2+1)  
depth = depth >> 1;  
end endfunction  
  
endmodule
```

# signed function

```
module top;  
...  
function signed [63:0] compute_signed  
(input [63:0] vector);  
...      // returned function value is signed  
endfunction  
  
...  
if (compute_signed(vector) < -3)  
begin ... end  
  
...  
endmodule
```